

guitar kill switch wiring diagram

****Guitar Kill Switch Wiring Diagram: A Guide to Adding Funky Stutter Effects****

guitar kill switch wiring diagram is a phrase that often pops up among guitar enthusiasts looking to spice up their sound with some unique stutter effects. If you've ever been captivated by the rhythmic chopping sounds popularized by rock and metal guitarists, you're likely curious about how to wire a kill switch into your instrument. This handy modification allows you to momentarily cut your guitar's signal, creating a distinctive "on-off" effect that can add tremendous character and versatility to your playing style.

In this article, we'll explore everything you need to know about installing and wiring a guitar kill switch. From understanding the basics of how it works, to exploring different wiring diagrams, and even some pro tips for customization, this guide should help you confidently add this feature to your guitar.

What Is a Guitar Kill Switch?

Before diving into the wiring diagrams, it's important to understand what a kill switch actually does. At its core, a kill switch is a simple on/off toggle or momentary switch that interrupts the signal path from your guitar's pickups to the output jack. When activated, it "kills" the sound, and when released, it restores the signal instantly. This creates a stutter or chopping effect, which can be used rhythmically to add flair to riffs, solos, and even ambient textures.

Unlike a traditional volume knob, which fades the sound gradually, a kill switch cuts the signal abruptly, creating a sharp, percussive effect. It's especially popular in genres like metal, punk, and experimental rock, but can be a fun addition to any player's toolbox.

Basic Components of a Kill Switch Wiring Setup

Understanding the parts involved helps make sense of any guitar kill switch wiring diagram. Here are the key elements you'll encounter:

- **Momentary Switch:** Usually a push-button switch that only stays engaged while pressed, ideal for quick "kill" effects.
- **Toggle Switch:** A switch that stays on or off until flipped again; less common but useful for different effect styles.

- **Pickup Output Wire:** The wire carrying the signal from the pickups to the output jack or volume control.
- **Ground Wire:** Essential for noise reduction and to complete the circuit properly.
- **Output Jack:** The guitar's connection point to the amplifier or effects chain.

Typically, the kill switch is wired in series with the pickup output, meaning it interrupts the signal path when activated.

How to Read a Guitar Kill Switch Wiring Diagram

A wiring diagram is essentially a visual map showing how all the components connect. When you look at a guitar kill switch wiring diagram, you'll notice:

- Lines representing wires connecting pickups, switches, and the output jack.
- Symbols for different components like switches (often a break in the line with a dot or arrow).
- Ground symbols indicating where connections are tied to the guitar's metal casing or a common earth point.

Most kill switch wiring diagrams are straightforward because the switch simply breaks or completes the circuit. However, the exact placement of the switch can vary depending on the guitar model and the effect you want.

Basic Wiring Diagram for a Momentary Kill Switch

Here's a simple outline of wiring a momentary kill switch:

1. Identify the hot wire from your pickup or volume pot output.
2. Cut this wire and connect one end to one terminal of the momentary switch.
3. Connect the other terminal of the switch to the output jack's hot terminal.
4. Ensure the ground wire from the pickup and output jack remains connected to the common ground.
5. When the switch is pressed, it breaks the connection, killing the signal.

This setup is often the easiest and most effective way to achieve the desired kill switch effect.

Advanced Kill Switch Wiring Diagrams and Variations

While the basic kill switch wiring is simple, many guitarists and tech-savvy players like to explore more intricate options:

Using a Toggle Switch for On/Off Kill

Instead of a momentary switch, a toggle switch allows you to turn the kill effect on or off, staying in the “kill” position until flipped again. The wiring is similar but designed to maintain the circuit break without holding the button.

Incorporating the Kill Switch with Pickup Selector

Some players wire the kill switch in conjunction with their pickup selector switch for more creative control. For example, wiring the kill switch to only affect the bridge pickup signal or to bypass the selector entirely when engaged.

Adding a Kill Switch to a Multi-Pickup Guitar

On guitars with multiple pickups, you can wire the kill switch to interrupt one pickup’s signal, the entire output, or even isolate certain pickups for selective muting. Wiring diagrams for these setups can be more complex but offer impressive tonal possibilities.

Tools and Materials Needed for Wiring a Kill Switch

Before starting your kill switch installation, make sure you have the following:

- Soldering iron and solder (preferably lead-free)
- Wire cutters and strippers
- Multimeter (useful for testing connections)
- Small screwdriver set

- Momentary or toggle switch (depending on your preference)
- Heat shrink tubing or electrical tape
- Replacement wire if needed

Having the right tools will make the process smoother and help avoid cold solder joints or wiring mistakes.

Step-by-Step Guide to Wiring a Kill Switch

If you're ready to get hands-on, here's a general process for wiring a kill switch into your guitar:

1. **Remove the guitar's backplate or pickguard:** Gain access to the control cavity where the wiring resides.
2. **Locate the hot wire:** This is usually the wire coming from the pickup selector or volume pot.
3. **Cut the hot wire:** Leave enough length on both ends to solder to the kill switch terminals.
4. **Solder the wires to the switch:** One wire to one terminal, the other wire to the opposite terminal.
5. **Mount the switch:** Drill a hole if necessary; position the switch where it's easily accessible during playing.
6. **Test the wiring:** Before reassembling, plug in your guitar and press the kill switch to ensure the sound cuts out and returns smoothly.
7. **Secure all components:** Use heat shrink or electrical tape to insulate solder joints and prevent shorts.
8. **Reassemble the guitar:** Put the backplate, pickguard, or control plate back on carefully.

Tips for a Successful Kill Switch Installation

- ****Use a high-quality switch:**** Cheaper switches may wear out quickly or produce scratchy sounds when engaged.

- ****Keep wiring neat:**** This reduces the risk of shorts and makes future repairs or modifications easier.
- ****Test thoroughly:**** Use a multimeter to check for continuity and ensure the switch breaks the circuit fully.
- ****Consider switch placement:**** Position the kill switch where it's easy to activate but not so close that you accidentally hit it during normal playing.
- ****Experiment with switch types:**** Some players prefer push-on/push-off switches for a different tactile feel.

Popular Kill Switch Wiring Diagram Variants Online

Many guitar forums and modding communities share free kill switch wiring diagrams. Some popular variations include:

- Series vs. parallel wiring: Changing how the switch interacts with pickups can create different tonal off effects.
- Kill switch with LED indicator: Wiring a small LED to show when the kill switch is active.
- Multi-function switches: Combining the kill switch with coil taps or phase switches.

Exploring these variations can inspire you to customize your guitar further, making your instrument truly one-of-a-kind.

Understanding the Impact of a Kill Switch on Guitar Tone

One common question among guitarists is whether adding a kill switch affects the overall tone or signal quality. When wired correctly, a kill switch simply interrupts the signal without altering tone when disengaged. However, poor solder joints, low-quality switches, or improper wiring can introduce noise or signal loss.

Keep in mind that the kill switch is primarily an effect tool rather than a tone modifier. It gives you rhythmic control over muting the signal, so it's best used as a creative addition rather than a replacement for tone shaping controls.

Incorporating a guitar kill switch into your instrument can open up exciting new sonic possibilities. Whether you're into the aggressive stutter effects of heavy metal or just want a fun way to spice up your playing, understanding the wiring and installation process is key. By following a clear guitar kill switch wiring diagram and taking your time with the setup, you can add this dynamic feature and start experimenting with fresh sounds right away.

Frequently Asked Questions

What is a guitar kill switch and how does it work?

A guitar kill switch is a device installed on electric guitars that allows the player to instantly cut off the signal output, creating stutter or rhythmic effects. It works by interrupting the electrical circuit between the guitar pickups and the output jack when pressed.

Where can I find a reliable guitar kill switch wiring diagram?

Reliable guitar kill switch wiring diagrams can be found on guitar DIY forums, manufacturer websites, and guitar electronics tutorial sites such as Seymour Duncan, StewMac, and various YouTube tutorial channels.

What components are needed to wire a kill switch in a guitar?

Typically, you need a momentary push-button switch (normally open), soldering tools, wires, and access to the guitar's output wiring (usually connected to the volume pot or output jack) to install a kill switch.

How do I wire a kill switch to a guitar with a single-coil pickup?

For a single-coil pickup, the kill switch is usually wired to interrupt the hot lead going from the pickup to the volume pot or output jack. When pressed, it grounds or disconnects the signal, cutting the sound. A wiring diagram specific to your guitar model is recommended.

Can a kill switch be wired without modifying the guitar's original wiring too much?

Yes, a kill switch can often be added with minimal modification by tapping into the wire leading to the output jack or volume pot. Using a momentary switch and careful soldering helps keep the original wiring intact.

What is the difference between a kill switch and a kill button in wiring diagrams?

In wiring diagrams, a kill switch is typically a momentary on/off switch that breaks the circuit when pressed, while a kill button may refer to a push-button switch. The terms are often used interchangeably, but the wiring method depends on the switch type.

Are there any common mistakes to avoid when wiring a guitar kill switch?

Common mistakes include wiring the switch incorrectly so it doesn't cut the signal, failing to ground the switch properly, and not using a momentary switch which prevents the kill effect from working as intended.

How do I test my guitar kill switch wiring after installation?

After installation, plug the guitar into an amplifier and press the kill switch. The sound should immediately cut off when pressed and return when released. If there is no change, check the wiring connections according to the wiring diagram.

Can I add a kill switch to a guitar with active pickups?

Yes, you can add a kill switch to guitars with active pickups, but wiring might be slightly different. It's important to ensure the switch interrupts the signal path correctly without affecting the battery power circuit. Consulting a wiring diagram specific to active pickups is recommended.

Additional Resources

Guitar Kill Switch Wiring Diagram: A Detailed Exploration for Tone Control and Performance

guitar kill switch wiring diagram serves as an essential reference for guitarists and technicians seeking to enhance their instrument's tonal capabilities and dynamic expression. The kill switch, a simple yet powerful modification, provides the ability to momentarily cut the guitar's signal, creating stutter effects, rhythmic muting, and innovative sound textures. Understanding the wiring diagram behind this feature is fundamental for anyone looking to install or troubleshoot this circuit on electric guitars.

This article delves into the nuances of guitar kill switch wiring diagrams, examining their components, variations, and practical applications. By exploring wiring schematics alongside performance considerations, guitarists

can make informed decisions about integrating kill switches into their setups.

Understanding the Guitar Kill Switch and Its Wiring

A kill switch is a momentary switch that interrupts the electrical signal from the guitar pickups to the output jack. Unlike traditional toggle switches that stay in a fixed position, the kill switch activates only when pressed or flipped, instantly silencing the guitar signal. This function enables players to produce rapid stutter effects or rhythmic cuts without adjusting volume knobs.

The wiring diagram for a guitar kill switch is straightforward but varies depending on the type of switch used and the guitar's existing electronics. Typically, the kill switch is wired in series with the hot wire running from the pickups to the output jack or the volume pot. When the switch is engaged, it shorts the signal path to ground, effectively killing the output.

Basic Kill Switch Wiring Diagram Components

- **Momentary Switch:** Usually a push-button or toggle switch designed to work only while pressed.
- **Hot Wire:** The signal-carrying wire from the pickups or volume pot.
- **Ground Wire:** Connects to the guitar's ground circuit to complete the kill action by shorting the signal.
- **Output Jack:** Where the signal leaves the guitar and is sent to an amplifier or effects chain.

Understanding each component's role helps in deciphering wiring diagrams and facilitates safe and effective installations.

Variations in Wiring Diagrams and Switch Types

Several types of kill switches are available, each requiring slightly different wiring approaches. The two most common switch types are:

1. Momentary Push-Button Switch

This switch only connects the circuit when pressed and immediately returns to the open position when released. The wiring diagram for this switch is minimal and usually involves wiring the hot wire through the switch to ground. This setup is favored for its tactile feedback and ease of use during live performance.

2. Toggle Switch (On-Off-On or On-Off)

Toggle switches offer more flexibility by maintaining the kill function in an “on” position without needing to hold the switch continuously. On-Off-On toggle switches can be wired to kill the signal or switch between pickups, adding versatility. Wiring diagrams for toggle switches are slightly more complex, often involving multiple wires and terminals.

Step-by-Step Guide to Wiring a Kill Switch

For those looking to add a kill switch to their guitar, a clear wiring diagram is critical. Here's a general step-by-step outline based on the most common push-button kill switch wiring:

1. **Identify the Hot Wire:** Locate the wire from the pickup selector or volume pot's output lug.
2. **Cut the Hot Wire:** Carefully cut this wire where the kill switch will be installed.
3. **Connect to the Switch:** Solder one end of the cut wire to one terminal of the momentary switch.
4. **Ground Connection:** Solder a wire from the other terminal of the switch to the guitar's ground circuit.
5. **Secure and Test:** Ensure all connections are insulated and secure, then test the switch functionality.

Following a well-documented wiring diagram reduces errors and ensures reliable operation.

Common Wiring Diagram Configurations

- **Series Kill Switch Wiring:** The switch is wired in series with the hot wire; pressing the switch shorts the signal to ground.
- **Parallel Kill Switch Wiring:** Less common, involves wiring the switch in parallel, interrupting the circuit differently.
- **Kill Switch with LED Indicator:** Some advanced wiring diagrams incorporate LEDs to visually indicate when the kill switch is active.

Each configuration offers different performance characteristics and may suit different player preferences.

Practical Considerations and Potential Drawbacks

While wiring a kill switch is relatively straightforward, several practical considerations should be acknowledged:

Impact on Guitar Tone

A kill switch, when wired correctly, has minimal impact on the guitar's tone when disengaged. However, improper wiring or poor solder joints can introduce noise or signal degradation. Using high-quality switches and components is advisable to preserve tonal integrity.

Durability and Reliability

Momentary switches are mechanical components subject to wear. Frequent use during performances can eventually cause switch failure. Selecting robust switch models and ensuring proper installation mitigates this risk.

Installation Complexity

In guitars with complex wiring schemes—such as those with multiple pickups and advanced switching options—integrating a kill switch requires careful planning. Consulting detailed wiring diagrams specific to the guitar model can prevent conflicts and ensure seamless integration.

Comparing Popular Kill Switch Wiring Diagrams

Various online resources and guitar modification manuals provide wiring diagrams tailored to different kill switch types. For example:

- **Seymour Duncan Kill Switch Diagram:** Focuses on a simple push-button switch wired to the volume pot's output for easy installation.
- **DIY Kill Switch Wiring for Stratocaster:** Often involves integrating the kill switch into the existing 5-way selector wiring, requiring more precise soldering.
- **Telecaster Kill Switch Wiring:** May involve bypassing the tone control or volume pot, depending on the player's preference.

Each diagram offers distinct approaches, and players should select one that aligns with their guitar's wiring layout and their desired kill switch functionality.

Enhancing Performance with Kill Switch Modifications

Beyond basic wiring, some guitarists explore advanced kill switch setups, such as:

- Dual kill switches for independent pickup muting.
- Combination kill switch and coil-splitting switches.
- Integration with MIDI or digital switching systems for complex performance control.

Such enhancements rely heavily on accurate wiring diagrams and a thorough understanding of guitar electronics.

The guitar kill switch wiring diagram remains a valuable tool for musicians and technicians aiming to push the boundaries of electric guitar sound. Whether for subtle muting effects or dramatic stutter performances, mastering the wiring intricacies ensures that the kill switch functions reliably and complements the instrument's tonal palette.

[Guitar Kill Switch Wiring Diagram](#)

Find other PDF articles:

<https://old.rga.ca/archive-th-091/Book?trackid=ovu45-8497&title=art-labeling-activity-anatomy-and-histology-of-the-thyroid-gland.pdf>

guitar kill switch wiring diagram: The Les Paul Manual Terry Burrows, 2015-12-15 Do you love Les Paul guitars? The Les Paul Manual: Buying, Maintaining, Repairing, and Customizing Your Gibson and Epiphone Les Paul has all you need to know about this amazing instrument.

guitar kill switch wiring diagram: The Stratocaster Manual Terry Burrows, 2015-11-26 This book is chock-full of great photos and details on buying and maintaining the legendary Fender Stratocaster, with Terry Burrows leading the way.

guitar kill switch wiring diagram: Electric Guitar Amplifier Handbook Jack Darr, 1971

guitar kill switch wiring diagram: Popular Science , 2002-12 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

guitar kill switch wiring diagram: Popular Science , 1945-08 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

guitar kill switch wiring diagram: Popular Science , 2004-12 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

guitar kill switch wiring diagram: Guitar Electronics Understanding Wiring Tim Swike, 2007-08-28 THIS IS THE ONLY WIRING GUIDE YOU WILL EVER NEED TO BUY. Learn step by step how to completely wire Telecaster, Stratocaster, Esquire, and Les Paul guitars and all of the potentiometers, capacitors, switches, ground wires, hot wires, pickups, output jack, and bridge ground. Even if you dont have a Fender or Gibson, this guide will teach you how to wire a guitar with 1, 2, or 3 pickups. Also learn where you can get the complete wiring kits for dirt cheap, and learn essential soldering tips. Why not learn how to change your pickups, tone or volume controls, switches, and capacitors yourself? There are a ton of modifications you can do to your guitar for dirt cheap. This book will also show you some secret hot rod techniques that the pros use. This book will teach you how to do coil tapping, coil cutting, phase switching, series wiring, parallel wiring, bridge-on switching, mini toggle switching, varitone switching, mega switching, yamaha switching, blend pots, and much more !!!

guitar kill switch wiring diagram: Beginner Intermediate and Advanced Hot Rod Techniques for Guitar a Fender Stratocaster Wiring Guide Tim Swike, 2008-03-21 IF YOU OWN A STRAT, THEN YOU NEED THIS BOOK! Learn step by step how to completely wire a Stratocaster and all of the potentiometers, capacitors, switches, ground wires, hot wires, pickups, output jack, and bridge ground. Even if you dont own a Fender, this guide will teach you how to wire a guitar with 1, 2, or 3 pickups. There are a ton of modifications you can do to your guitar for dirt cheap. This book will also show you some secret hot rod techniques that the pros use like: coil tapping, coil cutting, phase switching, series wiring, parallel wiring, bridge-on switching, toggle switching, mini toggle switching, varitone switching, mega switching, super switching, rotary switching, treble boost/solo switching, blend pots, push pull pots, stacked concentric pots, and much more !!! Plus you will learn everything you've ever wanted to know about 4-wire humbuckers that can fit into your standard

strat pickguard. Also includes audio files of the hot rod techniques.

guitar kill switch wiring diagram: *Making Guitar Pedals: Your First Pedal* Gerhard Wei\$, 2012-04-24 An absolute beginners guitar pedal guide. If you'd like to learn how to make a guitar pedal but have no idea how, then you've picked up the right guide. This book is a great way to get started in discovering a fun and highly rewarding pastime, even if you've no experience in electronics at all. We'll take you through all the steps of building your first guitar pedal from beginning to end including soldering school, case construction, and circuit making. Each section is filled with pictures and diagrams, so it's perfect for beginners. The pedal we'll be making is a killswitch pedal - a simple but ideal first pedal (plus it's cheap!). Worried you won't be able to find the parts? Don't stress: parts have been listed (along with part numbers) from shops based in the UK, USA and Europe. -- Publisher's website.

Related to guitar kill switch wiring diagram

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it

impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a

factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Guitar Emporium - The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Guitars in General - The Gear Page Poll Closed** One of you will get the guitar. Building thread. Thanks, Alexander Tone Volta. Alexander TVolt 24 25 26 Replies 519 Views 16K Today at 2:53 AM Alexander

Guitar Madness Pickups - The Gear Page They arrived a couple days after I ordered them. I installed them today and I am BLOWN AWAY. They sounded exactly like what I wanted-- more clarity and brightness than

The Gear Page The Gear Page is the leading online community and marketplace for guitars, amps, pedals, effects and associated gear

Any Sire guitar users here? - The Gear Page The tuning stability on the Sire is good. It's a factory guitar. It's better than the Fender due to having a bone nut and not a plastic one. Not that it impacts tuning stability, but the Sire locking

Do you actually wait 24 hours to open a guitar box after shipping? Seems like good practice if the box is super cold, but I've never waited. Got a guitar from SW 3 weeks ago, arrived in 70 degree temp. The note on the box almost pleaded to wait 24 hours

Guitar Emporium | Page 4 | The Gear Page The Gear Page takes no responsibility for transactions. Use appropriate judgment when buying or selling. Electric & Acoustic guitar ads ONLY!

Is there an absolutely stone cold certain method for aging chrome Discussion on methods for aging chrome-plated guitar hardware

GK Wireless system for Roland guitar synthesizers - The Gear Page I developed a wireless system for the GK divided pickup from Roland. It allows you to connect your guitar wirelessly to for example a GR-55. I have made

PSA: How to check guitar serial #s - The Gear Page The Gear Page is active on Facebook and Instagram! Follow us and see what great stuff we share from the community!

Back to Home: <https://old.rga.ca>